

DIGITAL LOGIC

RTL & VERILOG

Interview Questions

A Practical Study Guide
for Design Engineers

verilogcode.com

Copyright © 2015 by VerilogCode.com

All rights reserved. This book or any portion thereof may not be reproduced or used in any manner whatsoever without the express written permission of the publisher except for the use of brief quotations in a book review.

Ordering Information:

Quantity sales. Special discounts are available on quantity purchases by corporations, associations, and others. Orders by U.S. trade bookstores and wholesalers, please visit: www.VerilogCode.com

Printed in the United States of America

First Printing, May 2015

Revision 1.0

ISBN-13: 978-1512021462

ISBN-10: 1512021466


www.VerilogCode.com

For permission requests, contact VerilogCode.com

DIGITAL LOGIC

RTL & VeriLOG

Interview Questions

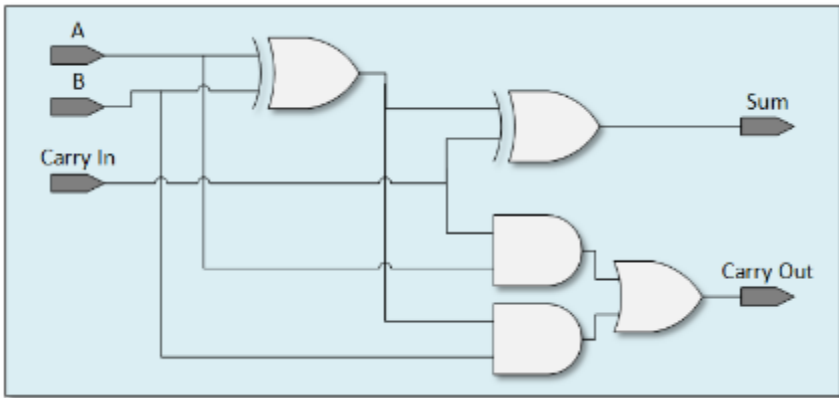

A Practical Study Guide for Design Engineers

verilogcode.com

DIGITAL LOGIC

RTL & VeriLOG

Interview Questions

About the Author:

Trey Johnson has been designing digital logic circuits and writing RTL code in both Verilog and VHDL languages for almost twenty years.

In the late 1990's, Johnson designed and developed some of the first multimedia hardware components used inside early smartphones, with his primary design focus in video and graphical subsystems, LCD and camera subsystems, and 2D hardware accelerators. He has worked closely and designed hardware components for both ARM and DSP processors and cache subsystems. He also has experience designing I/O peripherals such as resistive touch screen displays, magnetic card readers, PCI Express controllers and SerDes subsystems, and memory controllers.

Johnson has been granted three United States Patents for his digital design solutions. He is the founder of **VerilogCode.com** which is a website dedicated to sharing information about Verilog and RTL design.

Please visit the website for more digital design and job interview questions and to also share your own experiences.

This book is dedicated to Brandi, Tucker, Gunner and Alexa

*Thank you for riding with me on life's waves of change,
...and for embracing the journey along the way.*

Table of Contents

Introduction.....	17
RTL Verilog Syntax Questions	19
RTL Logic Design Questions	29
Clock Dividers, Clock Gating, and Reset Questions....	49
Clock Domain Crossing Questions	59
Power Related Design Questions	65
Digital Logic Questions	71
Logical Thinking Questions	93
Answers to Logical Questions.....	99
Further Reading and Studying on Your Own.....	103
Personal Interview Notes and Questions.....	105
Credit and Sources.....	119

List of Questions

RTL Verilog Syntax Questions

1. Explain *blocking* versus *non-blocking* statements
2. Show Verilog code for *bitwise* versus *conditional* operators
3. Verilog code for logic gates: *and*, *or*, *nand*, *nor*, *xor*, *xnor*
4. Verilog code for bitwise reduction
5. Verilog code multiplying and dividing by powers of 2
6. Verilog code for sign extension and concatenation
7. Write Verilog Code for *asynchronous* and *synchronous* Flip Flops
8. Verilog coding - what are three ways to code a mux
9. What type of circuit would the synthesis tool create for mux code
10. Verilog code for latch versus flip flop and draw timing diagram

RTL Logic Design Questions

11. Design a circuit to detect if a signal transitions in any direction
12. Design a circuit to detect a 1 cycle high pulse (synchronously)
13. Design a sequence detector circuit to detect 1,0,1,1,0 using FSM
14. Verilog code to detect a pattern 10110 anywhere in last 8 samples
15. For the timing diagram show, write Verilog code to create it
16. Design a debounce circuit to remove input glitches
17. Write Verilog code to convert BCD to gray code
18. Design a synchronous fifo module using dual port RAM
19. Design a circuit to detect if number is divisible by three
20. Design a circuit to calculate Fibonacci sequence
21. Design a circuit to find the maximum and second highest number
22. Design a circuit to output second, minute, and hour from 1ms input
23. Given the timing diagram, write the equivalent Verilog code
24. Draw the structure of a digital FIR filter with 5-taps

Clock Dividers, Clock Gating, and Reset Questions

25. Design a clock divide by 2 circuit
26. Design a clock divide by 3 circuit (with 50 percent duty cycle)
27. Design a clock divider by N circuit (with 50 percent duty cycle)
28. Design a glitch free clock gating cell with enable pin
29. How to detect a rising edge of an input signal if clocks are off
30. Design a reset circuit with async assertion and sync deassertion

Clock Domain Crossing Questions

31. What is metastability?
32. Design a circuit from a slow clock domain to a fast clock domain
33. Design a circuit to handle CDC from fast domain to a slow domain
34. How would the circuit change if you need to synchronize a bus?
35. Gray coding techniques to cross clock domains

Power Related Questions

36. Describe two components of power
37. Describe how to reduce static power
38. Describe how to reduce Dynamic power
39. Describe low power RTL coding techniques

Refresher: Digital Logic Questions

40. What is definition of setup and hold time for a flip flop
41. Venn Diagram and Boolean Logic
42. Logic Gate Design - Transistor Level
43. Cross Section of a transistor – understand the process node
44. Karnaugh Maps (clk divide by 3 circuit not 50-50 duty cycle)
45. Half Adder using XOR gates for addition and AND gate for carry
46. Using only 2 input muxes, create a *nand*, *nor*, *inverter*, *or*, *and*, *xor*
47. How to use and XOR gate like a controlled inverter?
48. Design an *inverter*, *and*, *or*, and *xor* gate using just nand gates
49. Create 4:1 mux using 2:1 mux
50. What is the fastest frequency this circuit can run?
51. Convert this decimal value to binary, hex, and octal format

Logical Thinking Questions

52. Four Gallons of Water
53. The Path to Freedom
54. Three Light Switches
55. Multiplication Question
56. Einstein's Riddle

List of Figures

1. Blocking Statements and Equivalent Gates (*Fig. 1*)
2. Non-blocking Statements and Equivalent Gates (*Fig. 2*)
3. Timing Diagram - capture with latch and flip flop (*Fig.3*)
4. Latch vs. Flip Flop timing diagram (*Fig. 4*)
5. Equivalent Gates from RTL code in Ex. 11 (*Fig. 5*)
6. Timing Diagram for Edge Detection using clocks (*Fig. 6*)
7. Sequence Detector using FSM (*Fig. 7*)
8. Decoder Circuit - Shift Register and Combinatorial Logic (*Fig. 8*)
9. Write the Verilog code to produce the above waveform (*Fig. 9*)
10. Classic Synchronizer Circuit using 2 Flip Flops (*Fig. 10*)
11. Circuit to detect low to high transition (*Fig. 11*)
12. BCD to Gray Code (*Fig. 12*)
13. Circuit to Generate Fibonacci Series (*Fig. 13*)
14. Write Verilog Code to Produce this Timing Diagram (*Fig. 14*)
15. 5-TAP Digital FIR filter (*Fig. 15*)
16. Timing Diagram for Clock Divide by 3 (*Fig. 16*)
17. Timing Diagram for Clock Divide by 3 (50-50 duty cycle) (*Fig.17*)
18. Timing Diagram for Clock Divide by 4 (50-50 duty cycle) (*Fig.18*)
19. Timing Diagram for Clock Divide by 5 (50-50 duty cycle) (*Fig.19*)
20. Latched Based Clock Gating Circuit (*Fig. 20*)
21. Classic 2-Stage Synchronizer (*Fig. 21*)
22. Clock Domain Crossing using Full Handshaking (*Fig. 22*)
23. Synchronize Bus Across Clock Domains Full Handshake (*Fig. 23*)
24. Example of Critical Path in Sequential Circuit (*Fig. 24*)
25. Venn Diagram (*Fig. 25*)
26. Logic Gates for $A \& (B|C)$ (*Fig. 26*)
27. Cross-section of CMOS Transistor (*Fig. 27*)
28. 3 State FSM for Clock Divider (*Fig. 28*)
29. Gray coding (with violation from state 11 to state 00) (*Fig. 29*)
30. 2-bit FSM (illegal gray code transition) (*Fig. 30*)
31. Six state FSM with correct gray code values (*Fig. 31*)
32. Equivalent Gates Result and Carry (*Fig. 32*)
33. Full Adder Circuit (*Fig. 33*)
34. Multibit Adder (*Fig. 34*)
35. Inverter (*Fig. 35*)
36. AND Gate Implemented with NAND Gates (*Fig. 36*)
37. OR Gate Implemented with NAND Gates (*Fig. 37*)

38. XOR Gate Implemented with NAND Gates (*Fig. 38*)
39. 4:1 Mux created with 2:1 muxes (*Fig. 39*)
40. 4:1 mux implemented with combinatorial logic (*Fig. 40*)
41. What is maximum frequency this circuit can run? (*Fig. 41*)

List of Verilog Coding Examples

1. Operator: & versus && (*Ex. 1*)
2. Operator: | versus || (*Ex. 2*)
3. Operator: ~ versus ! (*Ex. 3*)
4. Bitwise Operators (*Ex. 4*)
5. Bitwise Reduction (*Ex. 5*)
6. Shift Operations (*Ex. 6*)
7. Concatenation Operations (*Ex. 7*)
8. Verilog coding styles for a 4:1 mux (*Ex. 8*)
9. Priority Encoder (*Ex. 9*)
10. Parallel Muxing Scheme using full case statement (*Ex. 10*)
11. Verilog code for Latch and Flip Flop (*Ex. 11*)
12. Verilog Code for Edge Detection (*Ex. 12*)
13. Circuit to detect pulse (*Ex. 13*)
14. Example Verilog Code for *Fig. 9* waveform (*Ex. 14*)
15. Verilog Code for 3-bit Gray Code (*Ex. 15*)
16. Verilog code to convert BCD to Gray Code (*Ex. 16*)
17. FIFO control logic (*Ex. 17*)
18. FSM states for divisible by 3 circuit (*Ex. 18*)
19. Verilog code for Fibonacci Generation (*Ex. 19*)
20. Verilog code to generate one second, minute, and hour (*Ex. 20*)
21. Verilog Code for *Fig. 14* Timing Diagram (*Ex. 21*)
22. Verilog Code for Clock Divide by 2 (*Ex. 22*)
23. Verilog Code for Clock Divide by 3 with 50-50 duty cycle (*Ex. 23*)
24. Example Verilog Code for Generic Clock Divide by N (*Ex. 24*)
25. Example Verilog Code for Glitch Free Clock Gate (*Ex. 25*)
26. Asynchronous Edge Detection Circuit with no clocks (*Ex. 26*)
27. Verilog code for Reset synchronization (*Ex. 27*)
28. Start/Stop Conditions for Counters (*Ex. 28*)

List of Tables

1. Asynchronous versus Synchronous Flip Flops (*Table 1*)
2. Inverter Gate, Truth Table, and transistor-level circuit (*Table 2*)
3. NAND Gate, Truth Table, and transistor-level circuit (*Table 3*)
4. NOR Gate, Truth Table, and transistor-level circuit (*Table 4*)
5. AND Gate, Truth Table, and transistor-level circuit (*Table 5*)
6. OR Gate, Truth Table, and transistor-level circuit (*Table 6*)
7. Semiconductor Manufacturing Processing Nodes (*Table 7*)
8. Truth Table for an Adder (*Table 8*)
9. Inverter Implemented with 2:1 mux (*Table 9*)
10. AND Gate Implemented with 2:1 mux (*Table 10*)
11. OR Gate Implemented with 2:1 mux (*Table 11*)
12. NAND Gate Implemented with 2:1 mux and inverter (*Table 12*)
13. NOR Gate Implemented with 2:1 mux and inverter (*Table 13*)
14. XOR Gate Implemented with 2:1 mux and inverter (*Table 14*)
15. XNOR Gate Implemented with 2:1 mux and inverter (*Table 15*)
16. XOR Gate Used as Controlled Inverter (*Table 16*)
17. Path to Freedom Doors (*Table 17*)
18. Multiply Question (*Table 18*)

Introduction

I'm 30,000 feet above the ground, on a plane headed to San Diego for a job interview. I'm a little anxious, and I take some comfort in looking out of the small window pane next to me. My eyes wander back down to the magazine article sitting on my lap, then I read these words:

“Transitions. That’s all life is, and it’s tougher than physics. From school to work to retirement to dead”.

The magazine article is about children who are interviewing for preschool, and the most important characteristic that the administrators look for is how well can the child *adapt* to change with new surroundings and new rules. But this article could have been written about me: an engineer who spent eighteen years working for the same company, and one day was suddenly let go as a result of a corporate downsizing. I am now the one who must adapt to change, new surroundings, and new rules.

This book documents real interview questions that I encountered from my own personal job interviewing experiences with some of the top-tier semiconductor companies in the world. This book also contains fundamental digital design material and practical Verilog code examples that I created based on the themes from the types of questions that I experienced first hand. This book will help prepare you for your own interviewing process. It is by no means the end-all, but rather, consider this book as a great starting point. As you read through some of the questions, I will also share with you some of my personal insight and knowledge in the *Author’s Tips* section, which I have acquired through my career as a digital logic professional.

Interviewing for a job is like going on a date; at first you may feel a little nervous or awkward, but after some time and more interviews you soon become more comfortable and confident. Do not get discouraged in

the beginning! The job interviewing experience can be daunting. It will test your mental toughness. I experienced headaches during my first few interviews because of the long hours of mental stress. But the saying is true that *practice makes perfect*. After several more interview attempts, I became more comfortable, developed a sense of calmness, and felt more prepared to answer the questions.

I've encountered many different types of interview questions ranging from real world practical examples, to academic textbook or theoretical questions (usually asked by people with PHDs with not much practical experience), to tricky questions using some obscure circuit (which would never be applicable in the real world), to behavioral questions (usually asked by Human Resource representatives). This book focuses on real world practical examples, and it also discusses some of the tricky and obscure questions that are asked. Preparing for behavioral questions is important and is covered on our website.

This book is divided into multiple sections covering the following topics: RTL Verilog coding syntax, RTL Logic Design (including low power RTL design principles), clocking and reset circuits, clock domain crossing questions, digital design fundamentals, and logical thinking questions. Each section is unrelated to the other so you can jump around to any section or question that interests you.

This book is a great starting place for you to begin preparing for your job interview. This book provides you with a broad range of information and covers many topics. By the end of this book, you will have more knowledge and insight into the types of digital design interview questions being asked in the field of semiconductor digital design.


Remember that life will always bring about change, and it's how well you can transition and adapt that is important. Have a strong and positive attitude and you will succeed!

Good luck on your new journey!

RTL Verilog Syntax Questions

 
1. What is the difference between blocking and non-block statements, and when are they used?

Blocking statements are coded in Verilog with the = operator, and are used when creating combinatorial logic. This operator *blocks* the simulator from executing subsequent statements until the current evaluation and assignment is done. Consider the following code (E is assigned the immediate new value of C):



Blocking Statements and Equivalent Gates (Fig. 1)

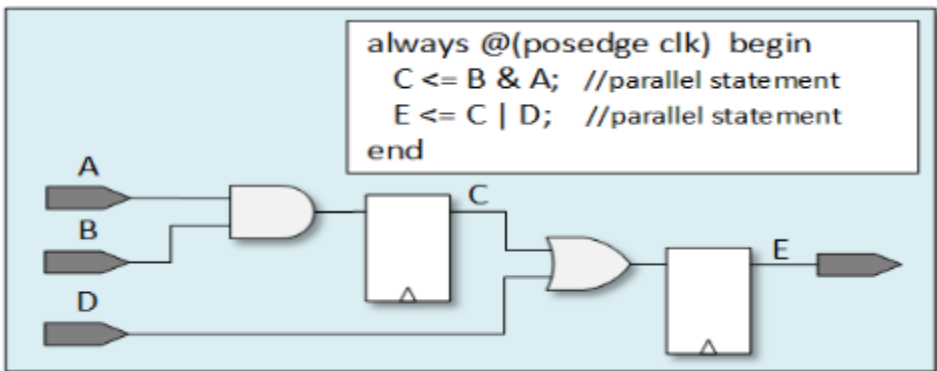Non-blocking statements are coded in Verilog with <= operator, are always used when coding flip flops inside a clocked process. The assignment is postponed until all the subsequent statements are evaluated. This allows for parallel or concurrent execution of statements. In this example, E is assigned the previous value of C (not the immediate):



Non-blocking Statements and Equivalent Gates (Fig. 2)

2. Explain the difference between logical and bitwise operators

In Verilog, you should understand the different syntax used for writing conditional if statement operations compared to writing code for creating logical gates with bitwise operations.

For bitwise operations resulting in an *AND* gate, use the `&` operator
assign C = A & B; //This will create an *and* gate

For conditional *and* if statements, use the `&&` operator
if (cond1 == 1'b1 && cond2 == 1'b1) {...}

Operator: `&` versus `&&` (Ex. 1)

For bitwise operations resulting in an *OR* gate, use the `|` operator
assign C = A | B; //This will create an *or* gate

For conditional *or* if statements , use the `||` operator
if (cond1 == 1'b1 || cond2 == 1'b1) {...}

Operator: `|` versus `||` (Ex.2)

For bitwise operations resulting in *inverter* gate, use the `~` operator
assign A = ~B; //This will create an *inverter*

For conditional *not* if statements, use the `!`
if (!cond1) { ... }

Operator: `~` versus `!` (Ex. 3)

3. Write code for logic gates: *and, or, xor, nand, nor, xnor*

```
assign C = (A & B); //AND gate
assign C = (A | B); //OR gate
assign C = (A ^ B); //XOR gate
assign C = ~(A & B); //NAND gate
assign C = ~(A | B); //NOR gate
assign C = ~(A ^ B); //XNOR gate
```

Bitwise Operators (Ex. 4)

4. How can you bitwise reduce a multibit signal?

```
wire [15:0] databus;
wire all_ones_detected;
wire is_databus_odd;
wire signal_not_zero;

assign all_ones_detected = &databus; // AND all the bits together;
assign is_databus_odd    = ^databus; // XOR all the bits together;
assign signal_not_zero   = |databus; // OR all the bits together;
```

Bitwise Reduction (Ex. 5)

5. What code multiplies or divides by powers of 2?

```
assign C = A << 2; // shift left ( multiply by 4)
assign C = A >> 3; // shift right (division by 8)
```

Shift Operations (Ex. 6)

6. How would you perform sign extension?

```
reg [4:0] A;
wire [9:0] C;
assign C = { {5{A[4]}} ,A}; // sign extension
```

Concatenation Operations (Ex. 7)

7. What are three ways to code a 4:1 mux in Verilog?

Assume the 4:1 mux inputs are named 'A, B, C, D', you will need a 2-bit *select* line (to choose between 4 inputs) and have a 1-bit *output*:

Coding Style 1:

```
assign output = (select == 2'b00) ? A :  
                (select == 2'b01) ? B :  
                (select == 2'b10) ? C : D;
```

Coding Style 2:

```
always @(*)  
if (select == 2'b00)  
    output <= A;  
else if (select == 2'b01)  
    output <= B;  
else if (select == 2'b10)  
    output <= C;  
else  
    output <= D;
```

Coding Style 3:


```
always @(*)  
case (select):  
    2'b00: output <= A;  
    2'b01: output <= B;  
    2'b10: output <= C;  
    2'b11: output <= D;  
end case;
```

Verilog coding styles for a 4:1 mux (Ex. 8)


You could also instantiate a mux cell directly if it exists in your library.

8. What circuit would synthesis create for previous mux coding styles?

Coding Styles 1 and 2 are equivalent circuits but use different coding styles, and both produce a priority encoder (path A is highest)

 Style 1: <pre>assign output = (select == 2'b00) ? A : (select == 2'b01) ? B : (select == 2'b10) ? C : D;</pre> Style 2: <pre>always @(*) if (select == 2'b00) output <= A; else if (select == 2'b01) output <= B; else if (select == 2'b10) output <= C; else output <= D;</pre>	Synthesis Results (Priority Encoder) 
--	---

Priority Encoder (Ex. 9)

 Style 3 <pre>always @(*) case (select): 2'b00: output <= A; 2'b01: output <= B; 2'b10: output <= C; 2'b11: output <= D; end case;</pre>	Synthesis Results (Parallel Case Mux) 
---	---

Parallel Muxing Scheme using full case statement (Ex. 10)


9. Write Code for Asynchronous/Synchronous Flip Flops and discuss the pros and cons of each

	Asynchronous	Synchronous
Verilog Code	<pre>always @(posedge clk or negedge rst) if (!rst) Q <= #1 1'b0; else Q <= #1 D;</pre>	<pre>always @(posedge clk) if (!rst) Q <= #1 1'b0; else Q <= #1 D;</pre>
Schematic		
Pros	No need for clocks to be running	No need to worry about asynchronous timing
Cons	Any glitch on reset signal will reset flops (If there are cross clock domain paths, then you need to synchronize the reset to each clock domain). Need to time the removal of reset	Need to time both the assertion of reset and also deassertion of reset

Asynchronous versus Synchronous Flip Flops (Table 1)

Author’s Tip: The questions so far has focused on Verilog syntax. Basic syntax questions can easily be looked up on Google ([after](#) you have a job), however, on a job interview it’s important to be prepared for these questions and knock them out of the park.

 10. Write Verilog to capture input below with a latch and a flip flop, and draw the timing outputs of each.




Timing Diagram - capture input into a latch and flip flop (Fig. 3)

```
//purposely coding latch
always @(clk or input)
  if (clk == 1'b1)
    Q_latch <= input;

//flip flop coding a Latch
always @(posedge clk)
  Q_flop <= #1 input;
```

Verilog code for Latch and Flip Flop (Ex. 11)

 The outputs of the latch and flip flop is below in the timing diagram:



Latch vs. Flip Flop timing diagram (Fig. 4)

The output of the flip flop only changes on the rising edge of clock, and will equal the value of the input captured at the rising edge of clock. The latch output will follow the input signal while the latch is open (in this case while clock is high). When the latch closes (clock is low), the output holds its previous value.

RTL Logic Design Questions

11. Design a circuit that can detect if an input signal transitions in either direction. Draw a timing diagram.


For this answer let's assume there is a clock available, and also the input signal D is on the same clock domain as our circuit. As with all interview questions, you should state your assumptions before answering the questions or confirm with the interviewer so you are both on the same page.

The easiest way to detect if an input signal has changed it simply compare current signal at time T to the previous version of the signal at time t-1. Therefore, a flip flop is used to capture the signal, and then you can compare it to the previous version of the same signal:

```
//capture the signal to have a delayed version
always @ ( posedge clk or negedge reset)
if (~reset)
    Q <= #1 1'b0;
else
    Q <= #1 D;


//detect signal transitions
assign Toggle = (Q ^ D) ; //xor gate
assign Falling = ~D & Q; //D is low, but was high
assign Rising = D & ~Q; // D is high, but was low
```

Verilog Code for Edge Detection (Ex. 12)

 

Equivalent Gates from RTL code in Ex. 11 (Fig. 5)

 The timing diagram is shown below. This waveform was drawn with tool called TimeGen, downloaded from XFusionSoftware.com:



Timing Diagram for Edge Detection using clocks (Fig. 6)

12. Design a circuit to detect a 1 cycle pulse input

Using delay states to remember the state of the signal for previous two cycles, you can simple check for 0, 1, then 0. You could also use an FSM.

```
//capture the signal and delay 2 cycles


always @ ( posedge clk or negedge reset)
if (~reset) begin
    Q1 <= #1 1'b0;
    Q2 <= #1 1'b0;
end
else begin
    Q1 <= #1 D; //delay T-1
    Q2 <= #1 Q1; //delay T-2
end;

assign pulse_high= ~D & Q1 & ~Q2;
```

Circuit to detect pulse (Ex. 13)

 13. Design a sequence detector for the pattern: 10110

One method is to design a FSM to detect the sequence. If the FSM reaches state 5, then generate a valid output pulse (all the other states will output low). It's also important to make sure you go back to correct state if the wrong value comes in (you don't always need to go back to idle state). You need to check if some of the sequence has already started and go back to the appropriate state.




Sequence Detector using FSM (Fig. 7)

 14. Detect if pattern 10110 appears in the last 5 inputs

To detect a pattern, we just need to design a decoder circuit. You could use shift registers and then add combinatorial logic to decode the string to check for a match. Whenever the values match, a pulse is generated. Be sure to clarify with the interviewer if the circuit needs to start over if the sequence is wrong (or if they want you to just detect anytime the pattern appears). If you need to detect the sequence, then you will need a state machine in the previous example.


The method below requires N number of shift registers to hold the length of the string or the sample window. Also, this circuit will always output true if the string matches.



Decoder Circuit - Shift Register and Combinatorial Logic (Fig. 8)

Author's Tip: Be sure to understand if the interview question requires a FSM or a simple decode. Also, how would you work the above example if the question changed to detect the pattern in the last 8 samples? The answer is to use a 8 bit shift register, and then decode for the appropriate sequence after output of each stage. Then you will need to logically or the outputs of each stage

 15. Given the timing diagram, write the Verilog code to produce the Start signal and the chip selects:



Write the Verilog code to produce the above waveform (Fig. 9)

```
//generate a counter to 3 (used to create start pulse)
always @(posedge clk or negedge rst)
    if (!rst)
        counter <= 2'b00;
    else if (counter == 2'b10)
        counter <= 2'b00;
    else
        counter <= counter + 1'b1;

assign start = (counter == 2'b01) ? 1'b1 : 1'b0; // start pulse

always @(posedge clk or negedge rst)
    if (!rst)
        cs <= 3'b000;
    else if (start == 1'b1)
        begin
            case (cs):
                3'b000: cs <= 3'b001;
                3'b001: cs <= 3'b010;
                3'b010: cs <= 3'b100;
                3'b100: cs <= 3'b000;
                default: cs <= 3'b000;
            endcase
        end


assign CS1 = cs[0]; assign CS2 = cs[1]; assign CS3 = cs[2];
```

Example Verilog Code for above waveform (Ex. 14)

16. Design a debounce circuit which removes glitches, with the following assumptions:

 
- 1) Assume the input signal is driven from an asynchronous clock.
- 2) Generate a pulse when the signal transitions from low-to-high.
- 3) The circuit should filter out any noise or glitches on the input signal. The input signal must be valid high for at least 2 clocks

Since the question said to assume the external input signal is driven from an asynchronous clock, the circuit we need to design must use a synchronizer on the input.



Classic Synchronizer Circuit using 2 Flip Flops (Fig. 10)

 After the synchronizers, the signal must be delayed two more cycles so we can check that it is still valid, and to also detect a rising edge.



Circuit to detect low to high transition (Fig. 11)

17. Write Verilog Code to generate a Gray Code counter

A valid question for a digital designer is to write RTL code to generate gray code. I've seen two ways to accomplish this. The first method is straightforward code without any tricks. The second method is a quicker method and something you should be aware to translate binary counter to gray code counter.

Below is RTL code written to generate a 3-bit gray code counter:

```
always @(posedge clk or negedge rst)
  if (!rst)
    counter <= #1 3'b000;
  else
    counter <= #1 counter + 1;
end

always @(counter)
  case (counter):
    3'b000 : gray_output <= 3'b000;
    3'b001 : gray_output <= 3'b001;
    3'b010 : gray_output <= 3'b011;
    3'b011 : gray_output <= 3'b010;
    3'b100 : gray_output <= 3'b110;
    3'b101 : gray_output <= 3'b111;
    3'b110 : gray_output <= 3'b101;
    3'b111 : gray_output <= 3'b100;
    default: gray_output <= 3'b000;
  end case;
```

Verilog Code for 3-bit Gray Code (Ex. 15)

One logical solution would be to create a 3-bit register and use it as binary counter that is incremented by 1 each clock cycle. A signal named “gray_output” decodes the binary counter and then generates the new gray code output. The problem with this approach is for a N-bit

counter you need to explicitly decode rite each state. A better, more generic solution using an XOR gate is presented below:

<u>BCD</u>	<u>Gray Code</u>	
0000	0000	
0001	0001	
0010	0011	
0011	0010	
0100	0110	
0101	0111	
0110	0101	
0111	0100	
1000	1100	
.....		
1111	1000	

BCD to Gray Code (Fig. 12)

```
always @(posedge clk or negedge rst)
  if (!rst)
    bcd_counter <= #1 4'b0000;
  else
    bcd_counter <= #1 bcd_counter + 1; // binary counter
end

//convert binary to gray code
assign gray_code = { bcd_counter[3] ,
                     bcd_counter[3] ^ bcd_counter[2],
                     bcd_counter[2] ^ bcd_counter[1],
                     bcd_counter[1] ^ bcd_counter[0]}
```

Verilog code to convert BCD to Gray Code (Ex. 16)

Author’s Tip: I was asked some variation of a gray coding question on 80% of my interviews. It is important in today’s low power design (since only 1 bit toggles saving dynamic power). Also, gray coding can be used to send a multi-bit vector across clock domains (after classic double synchronization).

18. Design a FIFO module that pushes and pops data using a dual port RAM. The FIFO logic should generate a fifo full signal and a fifo empty signal. (Assume both sides of FIFO are synchronous for write and read inputs)

Dual Port RAM datasheet

Inputs/Outputs: (inputs clk, rst, write, write_address, write_data, read_address; output read_data);

Description: : A dual port RAM allows both writes and reads to occur simultaneously to different address locations by using separate write and read address ports.

Writes: When the *write* signal is asserted high, data on the write_data bus is written into location pointed to by write_addresses.

Reads: The read address points to a location to retrieve the data on put onto the read_data bus.

Width x Depth: The RAM can store 256 entries

The code is listed below which generates the FIFO control logic:

```
module FIFO
input wire clk, rst, push, data_in, pop, data_in;
outputs fifo_full, fifo_empty, data_out;

reg[7:0] write_address;
reg[7:0] read_address;
reg[7:0] fifo_count;

//generate internal write address
always @(posedge clk or negedge rst)
if (!rst)
    write_address <= #1 8'b0000_0000; //256 locations
else if (push == 1'b1)
    write_address <= #1 write_address +1'b1;

//generate internal read address pointer
always @(posedge clk or negedge rst)
if (!rst)
```

```

    read_address <= #1 8'b0000_0000; //256 locations
else if (pop == 1'b1)
    read_address <= #1 read_address +1'b1;

//generate FIFO count
// increment on push, decrement on pop
always @(posedge clk or negedge rst)
if (!rst)
    fifo_count <= #1 8'b0000_0000; //256 locations
else if (push == 1'b1 && pop == 1'b0)
    fifo_count <= #1 fifo_count +1;
else if (push == 1'b0 && pop == 1'b1)
    fifo_count <= #1 fifo_count - 1;

//generate FIFO signals
assign fifo_full    = (fifo_count == 8'b1111_1111) ? 1'b1 : 1'b0;
assign fifo_empty   = (fifo_count == 8'b1111_1111) ? 1'b1 : 1'b0;

//Connect RAM
i_ram RAM ( .clk (clk), .rst(rst), .write(push),
.write_address(write_address), .write_data(data_in), .read_address
(read_address), .read_data(data_out));

```

FIFO control logic (Ex. 17)


Author's Tip: Note this solution presented uses a fifo count register (which adds another 8 registers) . Another method which saves area is to extend the write and read address pointers by 1 extra bit. When the pointers are equal, the fifo is empty. When the MSBs are different, but remaining bits[7:0] are equal, the fifo is full.

Also note that if this question used asynchronous clock domains, the circuit would need to synchronize any signals that cross domains such as fifo full or empty. But when you pass these signals across domains, the synchronization causes an extra delay (due to the sync flop) which would lead to overflows and underflows. To solve this, you can use gray coded write and read address pointers. The gray coded address pointers are then synchronized into the opposite clock domains, and then synchronously generates fifo_full and fifo_empty.

 19. Design a circuit to detect if a number is divisible by 3. The input to the circuit will be a single bit (either 0 or 1). Assume each input bit will be shifted into the LSB location. The output of the circuit should be 1 if the binary number received so far is divisible by 3.

The trick to this is to divide the binary number by 3 and then check the modulo value. The maximum number of states we could have based on the modulo results is just 3 (mod 0, mod 1, or mod 2).

Our FSM will start in state 0 which represents that the number is divisible by 3. If the modulo is 1, then we go to state 1. If modulo is 0, we go back to state 0 (and generate div_by_3 high). Each state represents the modulo value. For this example, let's assume the first input bit is 0, then 1, 1,0,1,0,0,1:



FSM states for divisible by 3 circuit (Ex. 18)

Author's Tip: You should practice other divisible values such as 4 or 5

20. Design a circuit to generate the Fibonacci series. The circuit should have an enable signal which allows the circuit to operate. When enable is low, the circuit should not advance to the next number.

By definition, the first two numbers in the Fibonacci sequence are 0 and 1, and the next number in the sequence is calculated by adding together the previous two numbers. For example: 0, 1, 1, 2, 3, 5, 8, 13,

Since the circuit must self generate the sequence, the design must have at least 2 registers to hold the starting numbers of 0 and 1.

```
//Define registers and signals
input wire clk, rst, enable;
output wire [31:0] sum;

reg [31:0] cur_num;
reg [31:0] next_num;


always @(posedge clk or negedge rst)
    if (!rst)
        cur_num <= #1 32'b0; //initialize to 0
    else if (enable == 1'b1)
        cur_num <= #1 next_num ;
end

always @(posedge clk or negedge rst)
    if (!rst)
        next_num <= #1 32'b1; //initialize to 1
    else if (enable == 1'b1)
        next_num <= #1 sum; //save the sum
end

//The output is the sum of the two numbers
assign sum = Q1 + Q2 ;
```

Verilog code for Fibonacci Generation (Ex. 19)

 Below is the equivalent block level diagram that illustrates what the previous Verilog code will create:



Circuit to Generate Fibonacci Series (Fig. 13)

For further preparation, you should try to convert other mathematical or computer science algorithms from software to a digital circuit.

Author's Tip: You should also understand the different tradeoffs and relationships between power, performance, and area when making decisions about the architecture of a digital circuit. That is, understanding the concept of getting better performance (by using parallel hardware which uses more area) compared to using least amount of gates (resource sharing) and doing things slower over more clock cycles.

21. Design a circuit to find the maximum value and the second maximum value from a group of binary numbers, using the least amount of comparators.

This question is slightly open ended (as some interview questions are) to see if you ask the right questions to solve the problem. Where are the group of numbers located? Do we need to fetch them first from memory with burst accesses? Is throughput and latency a concern?

If not, then all we need is one comparator and two storage registers (each with a reset value of 0) and then sequentially read and compare the incoming value against our currently stored values for top two numbers. We could resource share the comparator between the first and the second number before servicing the next value.

How could you find the maximum and second largest value the fastest way?

A faster method would be to do all the comparator operations in parallel using a binary tree, and use pipeline stages for faster bandwidth.

You could compare the first and second number and the winner would advance. In parallel the third and fourth numbers are compared and winner advances. Using this approach the maximum number will continue to the final pipeline stage. In parallel to the winner's bracket, you would need to also have a loser's bracket in order to find the 2nd largest number, but the same binary tree approach is applied.

Arthur's Tip: This follow up question really is testing if you understand the tradeoffs between performance and area (doing operations in parallel and pipelining) as opposed to doing it serially as the first question (less area but lowest bandwidth).

22. Design a circuit that will output 3 signals: second, hour, and minute. The circuit will receive an synchronous input signal that occurs every 1 ms.

```
//Define inputs
input clk, one_ms_pulse;
output reg second, minute, hour;

reg [9:0] ms_counter; //10 bit counter
reg [5:0] second_counter; //6 bit counter

always @(posedge clk or negedge rst)
    if (!rst)
        ms_counter <= #1 10'b0; //initialize to 0
    else if (one_ms_pulse == 1'b1) begin
        if (ms_counter == 999)
            ms_counter <= #1 10'b0; //reset to 0
        else
            ms_counter <= #1 ms_counter + 1'b1 ;
    end
end

always @(posedge clk or negedge rst)
    if (!rst)
        second_counter <= #1 6'b0; //initialize to 0
    else if (second == 1'b1) begin
        if (second_counter == 59)
            second_counter <= #1 6'b0; //reset to 0
        else
            second_counter <= #1 second_counter + 1'b1 ;
    end
end

always @(posedge clk or negedge rst)
    if (!rst)
        hour_counter <= #1 6'b0; //initialize to 0
    else if (second == 1'b1) begin
        if (minute_counter == 59)
```

(cont. on next page)

```


    minute_counter <= #1 6'b0; //reset to 0
else
    minute_counter <= #1 minute_counter + 1'b1 ;
end
end

assign second = (ms_counter == 999 && one_ms_pulse) : 1'b1 : 1'b0;
assign minute = (second_counter == 59 && second)      : 1'b1 : 1'b0;
assign hour    = (minute_counter == 59 && minute)      : 1'b1 : 1'b0;

```

Verilog code to generate one second, minute, and hour (Ex. 20)

 23. Given the timing diagram with input signals Clock and A, write Verilog code to produce output signal B.



Write Verilog Code to Produce this Timing Diagram (Fig. 14)

Judging from the output waveform B, when the input A when it is high the output follows it, but when the input falls the output is delayed by 1 cycle. The following code will produce the above timing diagram:

```

//flip flop to delay A input
always @(posedge clk or negedge rst)
    if (!rst)
        A_delay <= #1 1'b0;
    else
        A_delay <= #1 A;
assign B = A | A_delay ; //or gate


```

Verilog Code for Above Timing Diagram (Ex. 21)

 24. Design a 5-TAP FIR Filter and discuss an application

Digital filters can be used in various application such as audio or video processing. There are two types of digital filters FIR and IIR. The FIR circuit does not have any feedback, and it consists of multiply, add, and accumulate (MAC) function to generate the output. Each flip flop below represents a tap, and each tap is multiplied by its own coefficient and then summed together to create the output.

Upscaling (for example by 2), requires shifting in 1 value but then outputting 2 values. On the first cycle, one set of coefficients are loaded and then a MAC function is used to create first output value. On the next cycle, a 2nd set of coefficients are loaded and then MAC function outputs a 2nd value. The process repeats itself and the pipeline moves forward. The opposite is true for downscaling, in which the input rate is twice as fast as the output rate (shift in 2 values, but only output 1 value). This is a simplified explanation but now you an idea of how it is implemented.




5-TAP Digital FIR filter (Fig. 15)

Clock Divider, Clock Gating, and Reset Questions

 25. Write Verilog code for clock divide by 2 circuit

As a digital design engineer, you should understand how to code and design any clock divider circuit (both even or odd). Below is example of simple circuit for divide by 2:

```
//divide by 2 clock (toggle)
always @(posedge clk or negedge rst)
if (!rst)
    clk_div_2 <= #1 1'b0;
else
    clk_div_2 <= #1 ~(clk_div_2);
```



Verilog Code for Clock Divide by 2 (Ex. 22)

26. Clock Divide by 3 circuit with 50-50 duty cycle

For generating 50-50 duty cycle clock output for odd dividers, you will need to use both the *rising* edge and *falling* edges of input clock to produce the final generated output clock. Also, to guarantee glitch-free logic, the logic that drives the final output clock should guarantee (by design) that only 1 input signal to the combinatorial logic is changing at a time, and that input should be driven from a flip flop. Otherwise, you will create glitchy logic due to race conditions.

```
always @(posedge clk or negedge rst)
if (!rst)
    posedge_cnt <= #1 2'b00;
else if (posedge_cnt == 2'b10)
    posedge_cnt <= #1 2'b00;
else
    posedge_cnt <= #1 posedge_cnt + 1;
```

(cont. on next page)

```
always @(posedge clk or negedge rst)
```

(continued)

```
if (!rst)
```

```
    rise_pulse_reg <= 1'b0;
```

```
else if (posedge_cnt == 2'b01)
```

```
    rise_pulse_reg <= #1 1'b1;
```

```
else
```

```
    rise_pulse_reg <= #1 1'b0;
```

```
always @(negedge clk or negedge rst)
```

```
if (!rst)
```


```
    neg_pulse_reg <= #1 1'b0;
```

```
else
```

```
    neg_pulse_reg <= #1 rise_pulse_reg;
```

```
assign clk_output = rise_pulse_reg | neg_pulse_reg; //glitch free
```

 Verilog Code for Clock Divide by 3 with 50-50 Duty Cycle (Ex. 23)



Timing Diagram for Clock Divide by 3 (Fig. 16)

Author's Tip: For clock dividers with an *even divider* value, create a counter or FSM to toggle the output clock when the counter is half way. For *odd divider* values when duty cycle does not matter, just have one extra state where the clock is held high. For odd number dividers that require 50-50 duty cycle, it's very important to create a *glitch free* output.

27. Show Verilog code for clock divide by N circuit

```
reg [7:0] divider_value;           //software memory mapped register
                                   //(programmed to value minus 1 )

always @(posedge clk or negedge rst)
  if (!rst)
    posedge_cnt <= #1 {8{1'b0}};
  else if (posedge_cnt == divider_value)
    posedge_cnt <= #1 {8{1'b0}}; //reached end, start count over
  else
    posedge_cnt <= #1 posedge_cnt + 1;


always @(posedge clk or negedge rst)
  if (!rst)
    rise_pulse_reg <= #1 1'b0;
  else if (posedge_cnt == divider_value[7:1])
    rise_pulse_reg <= #1 1'b1; //set high (half way)
  else if (posedge_cnt == divider_value)
    rise_pulse_reg <= #1 1'b0; //set low (reached end)

//delay by half cycle (only for odd)
always @(negedge clk or negedge rst)
  If (!rst)
    neg_pulse_reg <= #1 1'b0;
  else if (divider_value[0] == 1'b0) // odd (since value minus 1)
    neg_pulse_reg <= #1 rise_pulse_reg;


assign clk_output = rise_pulse_reg | neg_pulse_reg;
```

 Example Verilog Code for Generic Clock Divide by N (Ex. 24)


There are waveforms on the next page which show clock divider values for divide by 3, divide by 4, and divide by 5.



 Timing Diagram for Clock Divide by 3 with (50-50 duty cycle) (Fig. 17)



 Timing Diagram for Clock Divide by 4 with (50-50 duty cycle) (Fig. 18)




Timing Diagram for Clock Divide by 5 with (50-50 duty cycle) (Fig. 19)

Author's Tip: Remember, it's important to understand why the odd clock divider circuits are glitch free. By our design, we are limiting only 1 input to the OR gate to change (and it is driven from a flop), otherwise glitches would occur. You should practice coding and drawing these timing diagrams on your own since these questions are popular on interviews.

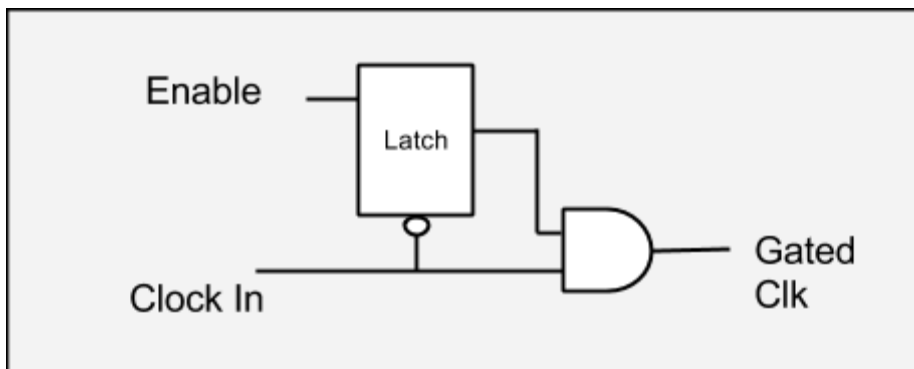28. Design a glitch free clock gating cell with enable

Understanding how to design a glitch free clock gate is important. The below diagram uses a falling edge latch to prevent glitches because the enable signal is not allowed to transition when the clock input is high:



Latched Based Clock Gating Circuit (Fig. 20)

If the latch was not there, then the enable signal could rise or fall while the clock is high, causing the gated output clock to glitch or have duty cycle less than 50%. The circuit works because when the input clock rises, the negative edge latch closes and doesn't allow the latch output to move (which keeps the enable signal to the AND gate stable even if the input enable signal moves). When the input clock falls, the latch is open and the enable signal is free to come across (since the input clock is low, it's ok now to gate the clock).

```
always @(clk, enable)
begin
    if (!clk)
        latch_q <= enable;
end

assign gated_clk = latch_q & clk_in;
```

Example Verilog Code for Glitch Free Clock Gate (Ex. 25)


There is an important timing constraint to understand with the

falling edge latch approach. The enable signal is usually launched on a rising clock edge, but the latch uses the falling edge to capture the enable signal therefore creating a true half cycle path. I've seen interview questions where it was asked why if you increase the clock frequency setup violations would appear in the clock gate. The answer is because of the half cycle path that exist between enable and falling edge latch.

 29. How to detect a rising edge of a signal if clocks are off?

If a local clock is currently not available to use, for example, if all the clocks are gated at the time, then you can use the input signal as the clock itself and directly connect it to clock pin of a flip flop. This will generate a level high signal that you can use to request for clocks. After the local clocks are up and running you still need to clear the flop, and you need to be careful with the timing and treat the output Q as asynchronous (therefore synchronize it before using it).

```
always @(posedge D or negedge clr)
if (!clr)
    Q <= #1 1'b0;
else
    Q <= #1 1'b1;
```



Asynchronous Edge Detection Circuit (when clocks are off) (Ex. 26)

30. Design a reset synchronizer circuit which allows asynchronous reset assertions, and synchronized reset de-assertions. The circuit receives clock and reset signal as inputs, and it must output a new reset output.

```
input rst, clk;
output local_reset;

reg reset_deassert_sync;
reg reset_deassert; //register for synchronous deassertion

always @(posedge clk or negedge rst)
if (!rst) begin
    reset_deassert_sync <= #1'b0;
    reset_deassert      <= #1'b0;
end
else begin
    reset_deassert_sync <= #1'b1; //could go metastable
    reset_deassert      <= #1 reset_deassert_sync; //sync flop
end

assign local_reset = rst & reset_deassert;
```

Verilog code for Reset synchronization (Ex. 27)


Clock Domain Crossing Questions

31. What is metastability?

Metastability occurs when a flip flop has a setup or hold time violation. The output of that flip flop becomes metastable, or enters a quasi-stable state, and it may settle either high or low. Metastability can have dangerous consequences if not handled properly in a design. First of all, all the timing paths inside a circuit should be checked for any setup or hold violations and be fixed. But in the case of clock domain crossings (CDC), metastability does occur and therefore special logic is needed for proper synchronization.

32. Design a circuit to synchronize a signal from a slow clock domain to a fast clock domain

Below is a common clock domain crossing circuit. If the source signal is from a slower clock domain, and if the destination clock domain is at least 2x faster, then you can use a classic 2-stage synchronizer:

 


Classic 2-Stage Synchronizer (*Fig. 21*)

Why are 2 stages needed? Since the Q1 output can become metastable (the source and destination clocks are asynchronous), a second stage is needed to allow the Q1 output to settle (either high or low). The Q2 output will be stable and can be used safely. STA tools will not time the path from source to Q1, but it is important to time the Q1 path to Q2 path.

 33. How would the previous circuit change if from a fast domain to a slow domain?

The circuit still requires a 2-stage synchronizer between the fast domain (source) and the slow domain (destination). However, the fast domain needs control logic to make sure the signal is held stable until the slow domain has a chance to synchronize it. This requires a full handshaking signal from the slow domain back to the fast domain (through yet another synchronizer) and only then is the fast domain allowed to clear Q0. Look at the schematic below:




Clock Domain Crossing using Full Handshaking (Fig. 22)

The control logic above is responsible for setting the Q0 flip flop to 1 and holding it steady until it sees the handshake (a rising edge pulse between Q4 and Q5), which indicates that the Q2 flop has captured the signal. The Q0 flop is cleared, but the control logic should prevent the setting of Q0 again until it sees a falling edge between Q4 and Q5 (which indicates that Q2 is low again) and the circuit can safely start over.

 34. How would you synchronize a data bus instead?

If you need to synchronize a multi-bit bus, you should not use a double flop approach on all of the bits as previously mentioned because some of the bits will make it in 1 cycle and some will make it across the domain in 2 cycles. Therefore a better approach is to only synchronize a 1-bit control signal to indicate to the other domain know that the bus is ready to be synchronized (that is, the bus is stable and will not change). The control signal should be synchronized and then used as a mux select to allow the bus to come across (otherwise the old value is held). Below is diagram of the circuit:



Synchronize Bus Across Clock Domains (Full Handshake) (Fig. 23)

35. Why are gray coding techniques are used for Clock Domain Crossings?

Gray coding by definition is a coding scheme where only 1 bit changes between states. Since only 1 bit is changing, then it is ok to synchronize a bus from one domain to another domain using just the normal classic synchronizer scheme. As you remember the problem with classic synchronization (double flop) across a bus is that some of the bits may transition before others (some flops would meet setup/hold condition) while others may not. But in the case where only 1 bit is changing, you don't have this issue.

One example of using gray coding with clock domain crossings is when designing an asynchronous FIFO. The fifo write address pointer is on one clock domain and the FIFO read address pointer is on the other domain. One technique is to use a gray coding scheme for each FIFO address pointer, and synchronize each of the pointers to the other domain and then generating the necessary control logic could be added to decide if FIFO has valid data, is full, or is empty.

Power Related Questions

36. Describe the two components that make up power

Low Power RTL design techniques are very important in today's digital logic designs because battery life is such an important role in mobile consumer electronics and in the future with wearables. The two components of power in digital circuits are *static* and *dynamic*.

37. Describe static power and how to reduce it in RTL

Static power, also known as leakage power, is directly related to the size or area of your design. The area is directly related to the number of logical gates (which are made up from transistors) created from your RTL code. When power is applied to the transistor, the transistors naturally leak current due to the manufacturing defects during the silicon process. In order to reduce static power, you can either minimize the number of gates in your design by resource sharing techniques (RTL coding), or by actually turning off the power to that logic.

Usually large sections of transistors are grouped together in their own power domain and a power controller is used to request power to be turned off or on depending if that logic will be needed. When sections are logic are powered down it is important that *isolation cells* are placed on all the outputs of the powered off circuits to ensure that a known value is driven after the gates are turned off. Isolation cells are special cells that could be instantiated in the RTL code (or inserted afterwards by a back end physical design team). It is important for the designer to make sure the isolation value that is driven (either iso high or iso lo cell) to inactive functional value (such as the reset value of the flop).

When power is turned off to the digital logic gates and registers, the values are lost. However, it may be desired for certain important control registers that you want to keep its value when power is turned off. There are special *retention flip flops* that can be instantiated in the RTL (if your library supports it) that will retain its value.

38. Describe dynamic power

Dynamic power is the power that is lost when a signal transitions from a logic high-to-low state or from a low-to-high state. This is due to the fact that in today's silicon circuits which use CMOS transistors, there is a current spike that occurs when the transistors are switching from an on to off state and there is a path (from VDD to GND). This is a direct result of the amount of transitioning and toggling of the signals inside your code.

39. Describe low power techniques with RTL code

Therefore, to lower the dynamic power in your digital design, your RTL code should avoid unnecessary toggling of signals. This can easily be accomplished with use of an enable signal. Your datapaths should always use enable signals when possible. Another example of using an enable is with counters. The below code that makes sure the counter doesn't toggle unless it's time to start and also it has a stop condition:

```
if (!rst)
    counter <= #1 {8{1'b0}};
else if (start_counter == 1'b1)
    counter <= #1 {8{1'b0}};
else if (counter < 8'b00101111)
    counter <= #1 counter + 1;
```

Start/Stop Conditions for Counters (Ex. 28)

By using enable signal, the flip flops will not toggle unnecessarily. Also, synthesis tools understand this and will gate the clock to the register for you automatically. These are considered leaf level clock gates.

The RTL design could also instantiate it's own clock gating cells at a middle level (above the leaf level). This can be useful when the designer knows that a group of logic will not be used unless it is enabled (for example perhaps a feature that software will enable during run time).

The RTL code would instantiate a clock gating cell (it is important that clocks are gated correctly and do not glitch. Refer to interview question about how to code a clock gating circuit). Be aware that you should not add a clock gate for a small number of flops (because adding more logic will increase the static power).

When trying to lower the dynamic power as much as possible, another method is to only toggle 1 bit of your FSMs as it transitions between states. This can be accomplished with gray coding for the state transitions. Gray coding can also be used in the read or write address busses that are connect internally to any FIFOs (or SRAMs) or address decoding logic.

Another example of less toggling is to use a databus inversion or databus encoding/decoding techniques. In some instances, if you have a wide databuses in your design and you want to reduce the amount of individual bit toggling, instead of driving each bit to its correct high or low value, it may make sense to instead drive a sideband signal called “inversion” that will let the receiver logic know that the databus has been inverted. This approach is used if the number of bits which are different between the current value and the next value of the databus are more than $N/2$ (where N is the width of the databus). Another technique which does not require the sideband signals is to encode the databus and decode it on the receiver side. There are plenty of white papers on this subject if you search on low power verilog databus encoding schemes.

As mentioned with static power reduction, if your design can reuse logic elements with resource sharing then it will also lower the dynamic power since less toggling through the gates.


Author’s Tip: this was a high level and introductory discussion on dynamic and static power. The subject is much deeper and if you are interviewing for low power design you should dive deeper into it.

Digital Logic Design Interview Questions

 40. What is definition of setup and hold time?

The setup time for a flip flop is the minimal amount of time its input signal must be arrive and be stable (not toggle) before its clock edge. Hold time is the minimal time after a clock rises that data must remain stable and not change (hold steady).

The most common reason setup times are violated is because there is too much logic between the launch flop and capture flop for the desired clock frequency to be met. The capture flip flop would have a setup time violation if the delay from the launch flop ($\text{clk} \rightarrow q + \text{wire delay} + \text{propagation delay through combo logic}$) was greater than the clock period.



Example of Sequential Circuit (Fig. 24)

There are multiple ways to fix setup violations. If it is early enough in the design cycle you could rewrite the RTL code (micro architect it in a different way). Or you could add a pipeline stage in the RTL path (break the path in the middle somewhere by adding another flop stage) and use an enable signal at the destination capture flop. Additionally the physical design team could resize the cells to have greater drive strength, or move the physical location of the cells closer to each other. And last resort, you could always run the clocks slower.

A hold violation is the opposite extreme of the above example. If there was no logic delay between the launch and capture flops, the signal may arrive too soon and cause a hold violation. To fix a hold violation, the physical design team would add delay in the paths (for example buffers).

41. Venn Diagrams and Boolean Logic


When I first started interviewing, I was hoping to rely on my practical work experience to get me through the job interview questions. I was quickly proven wrong. In fact, I was surprised on how ‘college’ like the questions were. For example, in practice we write RTL code (and don’t use Karnaugh maps anymore).

On one interview I was introduced to a senior design engineer. He asked me if I was a digital designer, and I nodded my head *yes*. He quickly followed up “then you shouldn’t have any problem solving a boolean logic and Venn diagram question”. *Huh?*

I thought to myself, *“Seriously? I’ve been designing digital circuits for eighteen years and never once did I need to draw a Venn Diagram or optimize boolean equations!”* That’s what the EDA tools are for.

Hoping he didn’t sense any discomfort or hesitation on my part, I quickly said that I haven’t done this since my digital logic classes in college. He seemingly didn’t care, and proceeded to draw on the whiteboard. He turned to me and asked:

 “What is the boolean equation for this shaded region below?”



Venn Diagram (Fig. 25)


I studied the diagram for couple of seconds, and mentally I could see it was made up of three intersections: $AB \parallel ABC \parallel AC$. I noticed that the middle cross section of ABC was redundant and was already covered by the other terms, so without thinking any longer I blurted out “ AB or’d with AC ”, and I wrote on the board: $AB \parallel AC$.

I also verbally pointed out that the middle cross section of (ABC) was redundant and already covered in my equation.

He nodded, and then asked me if I could simplify my equation even further. I looked at my equation again, and quickly answered, “yes, you can factor out the A ”, and then I wrote:

$$AB \parallel AC = A(B \parallel C)$$

 He then asked if I could draw the equivalent logic gates so I drew:




Logic Gates for $A \& (B \mid C)$ (Fig. 26)


Again, he gave a quick nod of the head for agreement. Then he asked if I could draw the transistor cell equivalent. I turned my head slowly and looked at him as if to ask “are you for real?” He responded that he just wanted to see how far I could go. I responded that once upon a time I could draw a CMOS inverter, and given some time I could probably figure out the other gates.

Author’s Tip: In reality, I should have been prepared for this question if I really wanted to impress him. On the next few pages, I’ve included the CMOS transistor level equivalent for the common digital logic gates. You should memorize all of these circuits and be prepared.

 
42. Transistor Level Equivalent of Digital Logic Gates



 
Inverter Gate, Truth Table, and transistor-level circuit (Table 2)



 NAND Gate, Truth Table, and transistor-level circuit (Table 3)



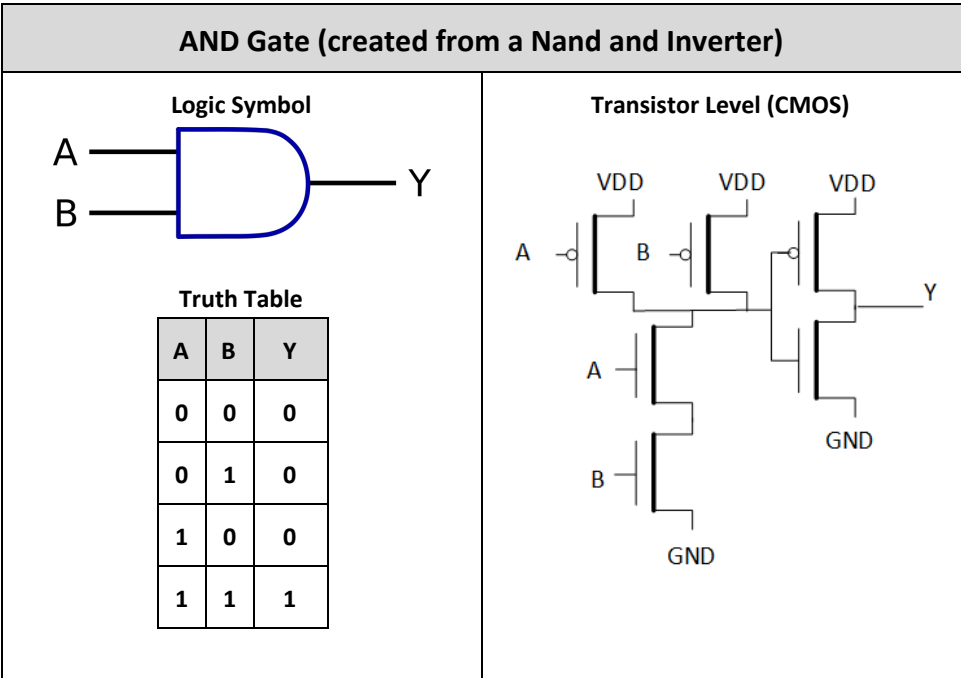
NOR Gate, Truth Table, and transistor-level circuit (Table 4)



AND Gate, Truth Table, and transistor-level circuit (Table 5)

OR Gate (created from a Nor and Inverter)


Logic Symbol

 

Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Transistor Level (CMOS)

 


OR Gate, Truth Table, and transistor-level circuit (Table 6)

 43. Cross section of a CMOS transistor

When I first started interviewing, I was not prepared for many of the academic questions since I had been out of school for many years. I always introduced myself as a front end RTL design engineer. Yet, I was still expected to know some fundamental concepts.

“So you would have a problem if I asked you to draw a cross-section of a CMOS transistor?”, asked one interviewer. I vaguely remembered details from my Semiconductor courses in college, but I restated that my primarily focus was writing Verilog code. This was obviously *not* the right answer! For reference, below is the cross-section of a CMOS transistor. I suggest simply memorizing it.



Cross-section of CMOS Transistor (Fig. 27)

Image from Wikipedia.org

You should also be familiar with process nodes and know in which technology nodes your designs were in. Refer to table below:

Year and Process		Year and Process		Year and Process	
1989	800 nm	2001	130 nm	2012	22 nm
1994	600 nm	2004	90 nm	2014	14 nm
1995	350 nm	2006	65 nm	2016	10 nm
1997	250 nm	2008	45 nm	2018	7 nm
1999	180 nm	2010	32 nm	2020	5 nm

Semiconductor Manufacturing Processing Nodes (Table 7)


44. FSMs, Karnaugh Maps and Gray Code

I've mentioned earlier in the book that I've been writing RTL code for almost 20 years, and not once did I need to draw a Karnaugh map. So I was a bit surprised with some of the interview questions that directly asked me to do so, and I was not prepared as I should have been.

I knew beforehand that I should study how to design clock dividers. Before the scheduled interview, I prepared to answer how to design any clock div N circuit with a 50% duty cycle. However, I wasn't prepared for any Karnaugh map questions!

The interviewer asked me to “design a clock circuit that divides by 3 using a FSM (finite state machine)”. He also stated that there was not a requirement for 50% duty cycle.

 This seemed simple enough and I said I would create a FSM with 3 states. As I drew the diagram on the whiteboard, he asked me to assign states values so I labeled them with binary values of “00”, “01”, and “10” respectively:



3 State FSM for Clock Divider (Fig. 28)


He nodded in agreement, but then asked me to change the state values that I assigned to instead use gray coding. I understood that Gray coding has rules and that only 1 bit could change between each state transition. So I relabeled the states just as he asked, with the following values: 00, 01, 11. As soon as I assigned the last state, I realized there

would be a problem going from the last state back to the first state since two bits changed, violating Gray code rules.



Gray coding (with violation from state 11 to state 00) (Fig. 29)

This is where I got stuck (and, then nervousness set it). After some time, he asked me to draw a Karnaugh map for the state values. At this point of the interview, I really felt I was following a rehearsed script, like he had asked this question hundreds of times before, and he just wanted to see how my thought process would work as we worked through this together. Below is the Karnaugh map I drew for my FSM:

 


2-bit FSM (illegal gray code transition) (Fig. 30)

Clearly from the low state 11 it is illegal to go back to high state 00. From the diagram above, there is an empty slot (state 10) which is available which could be used to generate a high output. If you were to use this unused stated, then the FSM could reverse and go back to two previous low states, but that would require extra control logic (flags) to be

set. It did not occur to me at the time to suggest that solution.

Also, he reminded me, that Karnaugh maps squares are structurally already gray coded, that is, each adjacent square in a Karnaugh map (above or below, or left or right) is a valid gray code transition. This is a very important fact to remember that I had forgotten my college classes.

 After some discussion with the interviewer, I finally deduced that I could use a 3-bit state value for the FSM, and he asked me to draw a new Karnaugh map to represent the new states. I decided to use the following states and start in the upper left corner: 000 (high), 001 (low), 011 (low), then 111 (high), 101 (low), and 100 (low):



Six state FSM with correct gray code values (Fig. 31)

The key to solving this question is remembering that when using Karnaugh maps you can move freely around adjacent state spaces with only a 1-bit change in value. By moving around the states, you can piece together the answer. In fact, any six states will work as long as you circle back to the beginning. After this interview, I decided to dig further into Gray coding since I recognized a trend. Gray coding started to become a recurring theme in my interviews for low power digital design.

Gray coding techniques are discussed in other questions in this book with some possible use-case scenarios.


45. Half Adder using XOR gates and AND and OR gates

A basic question and concept that you should understand is how to design digital logic for adders. Below is the truth table, K-map, and logic implementation:


A	B	Result	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Truth Table for an Adder (Table 8)

 
Karnaugh Map for the Result and Carry bits:



 Result = $\overline{A} B + \overline{B} A$
= A XOR B




Carry = A AND B

 


Half Adder (Fig. 32)

 By placing two half-adders together you can create a full adder circuit:



Full Adder Circuit (Fig. 33)

 Placing multiple 1-bit full adders together and you can get a multibit adder. Below is a 4-bit adder:




Multibit Adder (Fig. 34)

Author’s Tip: It is important to understand how these basic building blocks are used together just in case you are asked. It is too easy as a front end designer just to type in verilog: $R = A + B$; Now you will have understanding what’s happening in the synthesis tool.

 46. Creating digital logic gates using 2:1 mux


You'll be surprised to know that these following questions appear more often than not. I consider them tricks, and they are no way practical at all. However, it does make you understand the truth table of the common gates and also are logical once you understand you can use VDD and GND when you construct the circuit. You need to create all the logic gates using a 2-input mux. I suggest you just memorize this.



For an *inverter*, you should connect the A input to the select line ($A=S$)

A	Y
0	1
1	0

 
Inverter Implemented with 2:1 mux (Table 9)



For an *AND* gate, you connect the A input to the select line ($A=S$)

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 AND Gate Implemented with 2:1 mux (Table 10)




For an *OR* gate, you connect the A input to the select line ($A=S$)

A (S)	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

OR Gate Implemented with 2:1 mux (Table 11)

 
To create a NAND or NOR gate, you could place an inverter on the output of and AND or OR gate. Another method is presented below in which you could invert the A or B input and then use the 2:1 mux implementation below:



For an *NAND* gate, you connect the B input to the select line ($B=S$), and then use A' (not A)

A	B (S)	Y
0	0	1
0	1	1
1	0	1
1	1	0

 NAND Gate Implemented with 2:1 mux and inverter (Table 12)




For an *NOR* gate, you connect the A input to the select line ($A=S$), and then use B' (not B)

A (S)	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

NOR Gate Implemented with 2:1 mux and inverter (Table 13)

 Along with an inverter, you could also create an XOR gate with 2:1 mux:




For an *XOR* gate, you connect the A input to the select line ($A=S$)

A (S)	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

XOR Gate Implemented with 2:1 mux and inverter (Table 14)

 And for completeness, the XNOR gate with 2:1 mux and inverter is included here:




For an *XNOR* gate, you connect the B input to the select line ($B=S$)

A	B(S)	Y
0	0	1
0	1	0
1	0	0
1	1	1

XNOR Gate Implemented with 2:1 mux and inverter (Table 15)

 47. How do you use and XOR gate as a controlled inverter?




When *control* is 0, the A input passes through. When control is 1, the A input is inverted.

Control	A	Y
0	0	0
0	1	1
0	0	1
1	1	0


XOR Gate Used as Controlled Inverter (Table 16)

 48. Design an *inverter*, *and*, *or*, and *xor* gate using only nand gates


I'm not sure why these questions are asked, since they are not practical. But, here are some common solutions to creating other gates with just nand gates.




Inverter (Fig. 35)

 

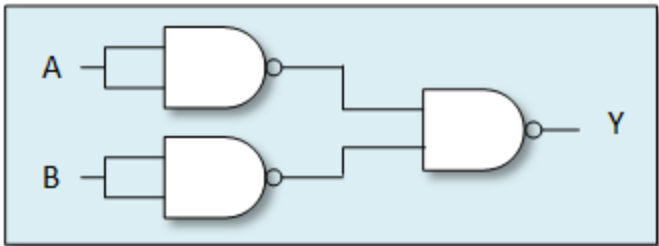AND Gate Implemented with NAND Gates (Fig. 36)




 OR Gate Implemented with NAND Gates (Fig. 37)




XOR Gate Implemented with NAND Gates (Fig. 38)

49. Create a 4:1 Mux using 2:1 muxes

 

4:1 Mux created with 2:1 muxes (Fig. 39)


Above is the basic circuit, but if you dig in further and look at the logic gates, here is a 4:1 mux with purely combinatorial logic:

 

Example 4:1 mux implemented with combinational logic (Fig. 40)

 50. Frequency, Period, and Propagation Delay

Assuming propagation delay through each gate below is 1 ns, what is the maximum frequency this circuit can run?



What is maximum frequency this circuit can run? (Fig. 41)

Frequency = $1 / T$. The maximum frequency is directly related to worst total path in the circuit. In this example, the worst path is a 3 gate delays starting from point A through the *XOR* gate, then *AND* gate, then the *OR* gate for a total path delay of 3 ns. Therefore, the safest (fastest) frequency is 333.33 megahertz ($1/3$ ns).

Author's Tip: As a reminder, there are 4 possible timing groups in a given module: input port to output port, input ports to internal flop, internal flop to internal flop, and internal flop to output port.

Remember that in a real silicon circuit, there are also wire delays associated with the signals. In addition, each of the inputs will have some an input delay associated with them (even if they are driven from flops there is a clock to Q delay before the signal becomes available and routing). For output ports, keep in mind there is a capture flop on the other end so you must meet the setup time requirement of the capture flop.

51. Convert decimal value 13 to binary, hex, and octal

There is nothing tricky about this problem. It is straightforward but some people have issues for the conversion to octal (if they haven't done it in a long time). Given the decimal value 13, the binary equivalent is 1101, the hex value is D, and the octal value is 15.

Logical Problem Questions

When I'm traveling for a job interview and have some spare time to pass, I like to entertain myself by working logical puzzles. Logic puzzles can help stimulate your brain.

They may not seem related to digital design at first, but they do require logical thinking to solve them (which is the basis of engineering). Whether these types of problems detect if a candidate would be a good employee or not is arguable. I think that it is better to be prepared in case these types of questions are asked. Some of my colleagues have been asked these types of questions or variations of them.

The questions listed in this section were found on the internet just by searching for logic puzzles. I selected a few that do not have trick answers or tricky wording. I've only included questions that have logical solutions. Also, I did not include any intensive math related questions or any that require advanced mathematical calculations. Instead, these questions involve straightforward logical thinking and problem solving skills.

52. Four Gallons of Water

Using just a 5 gallon bucket and a 3 gallon bucket, how can you measure exactly four gallons of water in the 5 gallon bucket? (Assume that you have an unlimited supply of water and that there are no measurement markings of any kind on the buckets.)

53. The Path to Freedom

You are a prisoner in a cold dungeon. After a long search you discover three doors. Behind only one of the doors lies the path to freedom. Behind the other two doors, however, is not the path to freedom (you can assume some violent death ensues...)

There are different inscriptions on each door, labeled as followed:

Door 1	Door 2	Door 3
This door leads to freedom	This does does not lead to freedom	The middle door does not lead to freedom

Path to Freedom Doors (Table 17)

Given the fact that at *least one* of the three statements on the three doors is true and at *least one* of them is false, which door would lead you to freedom?

54. The Three Light Switches

There are three light switches in your basement. All of them are currently in the off position. Each switch controls its own lamp on the floor above. You need to find out which light switch controls which lamp. You are not allowed to break walls or inspect wiring of circuits, etc.

You must start in the basement where the three light switches are location. You may turn on or off the switches any number of times, but you may only go upstairs one time to inspect the lamps (and at that time you must make your decision). How can you determine which switch controls each lamp with only one trip upstairs? *Hint: you will need to think outside the box for this one.*

55. Multiply Question

ABCD x 9 ----- DCBA	What are the values for A,B,C,and D? (Each variable represents a <i>different</i> single digit value between 0 and 9)
---	---

Multiply Question (Table 18)

56. Einstein's Riddle

There are 5 houses in 5 different colors in a row. In each house lives a person with a different nationality. The 5 owners drink a certain type of beverage, smoke a certain brand of cigar, and keep a certain pet. No owners have the same pet, smoke the same brand of cigar, or drink the same beverage. Other facts:

1. The Brit lives in the red house.
2. The Swede keeps dogs as pets.
3. The Dane drinks tea.
4. The green house is on the immediate left of the white house.
5. The green house's owner drinks coffee.
6. The owner who smokes Pall Mall rears birds.
7. The owner of the yellow house smokes Dunhill.
8. The owner living in the center house drinks milk.
9. The Norwegian lives in the first house.
10. The owner who smokes Blends lives next to the one who keeps cats.
11. The owner who keeps the horse lives next to the one who smokes Dunhill.
12. The owner who smokes Bluemasters drinks beer.
13. The German smokes Prince.
14. The Norwegian lives next to the blue house.
15. The owner who smokes Blends lives next to the one who drinks water.

Question: Who owns the fish?

LOGICAL PROBLEMS (Answers)

52. Four Gallons of Water

ANSWER:

1. Fill up the 5-gallon bucket.
2. Pour the contents of this into the 3-gallon bucket. You are now left with two gallons of water in the 5-gallon bucket.
3. Dump out the water in the 3-gallon bucket.
4. Pour the two gallons of water that are in the 5-gallon bucket into the 3-gallon bucket.
5. Fill up the 5-gallon bucket up again.
6. Top off the 3-gallon bucket with water from the 5-gallon bucket leaving you with 4 gallons of water in the 5-gallon bucket.

ALTERNATE ANSWER:

1. Fill the 3-gallon bucket.
2. Pour the 3 gallons of water into the 5-gallon bucket
3. Fill the 3-gallon bucket again.
4. Fill up the 5-gallon bucket with the 3-gallon bucket, leaving you with 1 gallon left in the 3-gallon bucket.
5. Empty out the 5-gallon bucket.
6. Pour the remaining 1 gallon of water from the 3-gallon bucket into the 5-gallon bucket.
7. Fill the 3-gallon bucket.
8. Pour the 3 gallons of water from the 3-gallon bucket into the 5-gallon bucket leaving you with 4 gallons of water in the 5-gallon bucket.

53. The Path to Freedom:

ANSWER:

1. Assume Freedom is behind the first door. All three doors would then have true statements which we know is not possible since one of them must be false.
2. Assume Freedom is behind the second door. All three doors would then have false statements which we know is not possible since

one of them must be true.

3. Freedom is therefore behind the third door. The blue door and the green door have true statements and the red door has a false statement.

54. The Three Light Switches

ANSWER: Turn Switch 1 on and leave it on for a little while... about five minutes or more... and then turn it off. Turn Switch 2 on and go upstairs to inspect the lamps.

- The lamp with the bulb that is *off* but still *warm* is controlled by Switch 1.
- The lamp that is currently *on* is controlled by Switch 2.
- The lamp that is *off* and *cold* is controlled by Switch 3.

55. The Multiply Question

ANSWER: $1089 * 9 = 9801$ A=1, B=0, C=8, D=9

56 Einstein's Riddle

ANSWER

The German sits in his Green House, smoking his Prince cigars, drinking coffee, and watching his FISH.

The rest go like this-

1st House: Yellow, Norwegian, Water, Cats, Dunhill

2nd House: Blue, Dane, Tea, Horse, Blends

3rd House: Red, Brit, Milk, Birds, Pall Malls

4th House: Green, German, Coffee, FISH, Prince

5th House: White, Swede, Beer, Dogs, Bluemasters

Further reading and studying on your own...

This book attempts to focus on the front end RTL and Verilog interview questions. However, there are so many other topics which were not covered. You should continue to research and study on your own for these topics, or visit the website for information: **www.VerilogCode.com**

Verification

- What are the differences between SOC level and IP level testing
- Differences between writing CPU compiled tests in C or assembly compared to unit level testing using constrained random tests
- Defining test plans and functional testing requirements
 - writing functional cross coverage buckets
- Measuring code coverage
 - line, branch, condition, and toggle coverage

DFT (Design For Test)

- Understand scan flops and basics about how scan chains work
- Understand test modes for clock gating cells, latches (make them transparent), and memory (drive inputs to the outputs)
- Understand memory BIST or PBIST testing

Physical Design Questions

As a front end RTL designer, you may not be familiar with STA or the physical design flow. However, you should be aware of what physical designers can do, and what methods and tools that they use. Including:

- Give an example of what is included in a synthesis constraint file
- If STA results are clean, but the netlist and sdf files are showing Xs in gate level simulations, what could be the possible causes?
 - incorrect constraint files
 - the physical placement (location) of cells

- clock domain crossings
- Understand some ways physical design can fix setup and hold violations, by:
 - Replication of logic
 - Resizing cells
 - Moving logic from right to left side
 - Breaking paths (pipeline techniques)
 - Under (PVT) relationships: Power, Voltage and Temperature
- Understand Dynamic Frequency Voltage Scaling

Personal Interview Notes and Questions

Use these next pages for your own personal interview notes and experiences. As soon as you finish an interview, you should write down the questions immediately before you forget them. These pages can be used as your personal journal that you can review before each interview.

From my experience, if you immediately write down the questions and then review all of them before your next interview then you become more and more comfortable answer questions.. And chances are you may hear a related question on your next interview. It also builds up your confidence and library of information.

Personal Interview Notes and Questions

Personal Interview Notes and Questions

Personal Interview Notes and Questions

Personal Interview Notes and Questions

Personal Interview Notes and Questions

Personal Interview Notes and Questions

Personal Interview Notes and Questions

Personal Interview Notes and Questions

Personal Interview Notes and Questions

Personal Interview Notes and Questions

Personal Interview Notes and Questions

Personal Interview Notes and Questions

Personal Interview Notes and Questions

Credits and Sources

Websites Sources:

<https://en.wikipedia.org/wiki/CMOS>

<http://www.design-reuse.com/articles/20775/hdl-design-low-power.html>

<http://www.asic-world.com>

<http://6004.mit.edu/Fall14/tutprobs/fsm.html>

White Papers:

OSR Journal of VLSI and Signal Processing (IOSR-JVSP). ISSN: 2319 – 4200,
ISBN No. : 2319 – 4197 Volume 1, Issue 3 (Nov. - Dec. 2012), PP 32-37
Asynchronous FIFO Design with Gray code Pointer for High Speed AMBA AHB
Compliant Memory controller G.Ramesh, V.Shivaraj Kumar, K.Jeevan Reddy

Clock Dividers Made Easy by Mohit Arora. www.mikrocontroller.net

People

I would like to thank and acknowledge the following people who helped me during my professional career, and also helped me to prepare for my own job interviewing experience and preparation: Atif Hussain, Rajitha Padakanti, Bob Mizell, and William Wallace

Places

I would like to thank the Red Horn Coffee House and Brewing Co. in Cedar Park, TX for providing Wifi internet access. I was able to finish this book while enjoying some of the best coffee and craft beers.